

## Homework 2 Virtuoso Questions

2.4

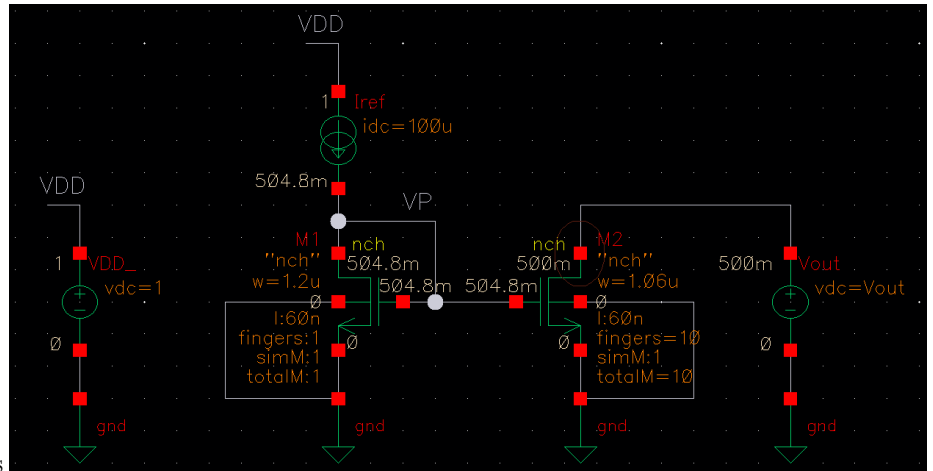


fig.(a) widths and lengths

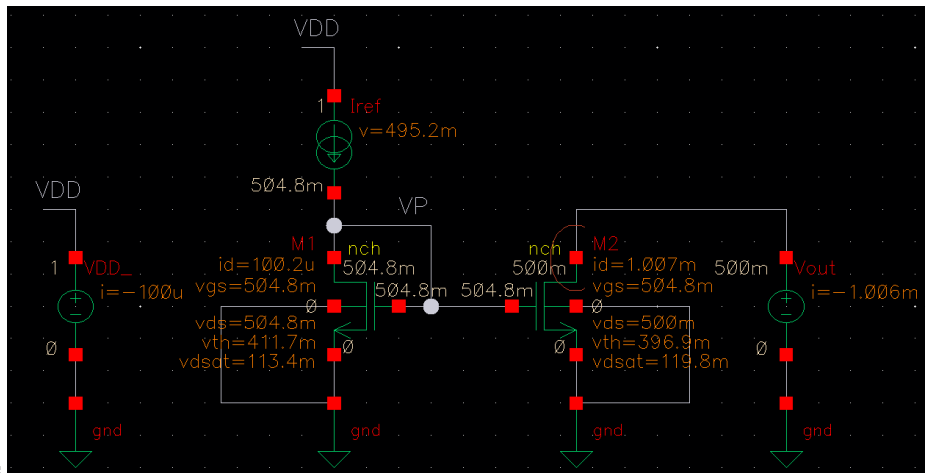


fig.(a) operating points

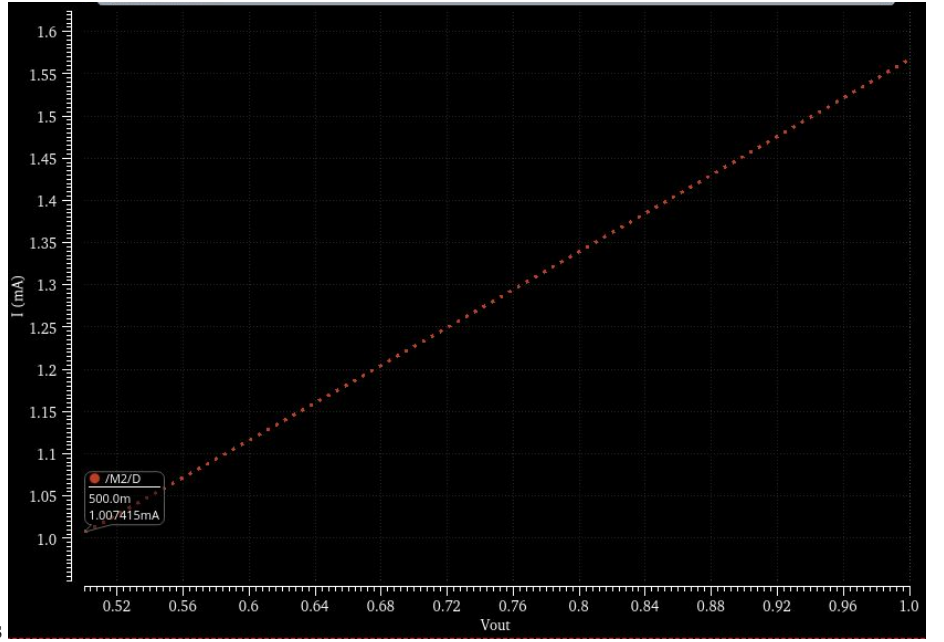


fig.(a) simulation results

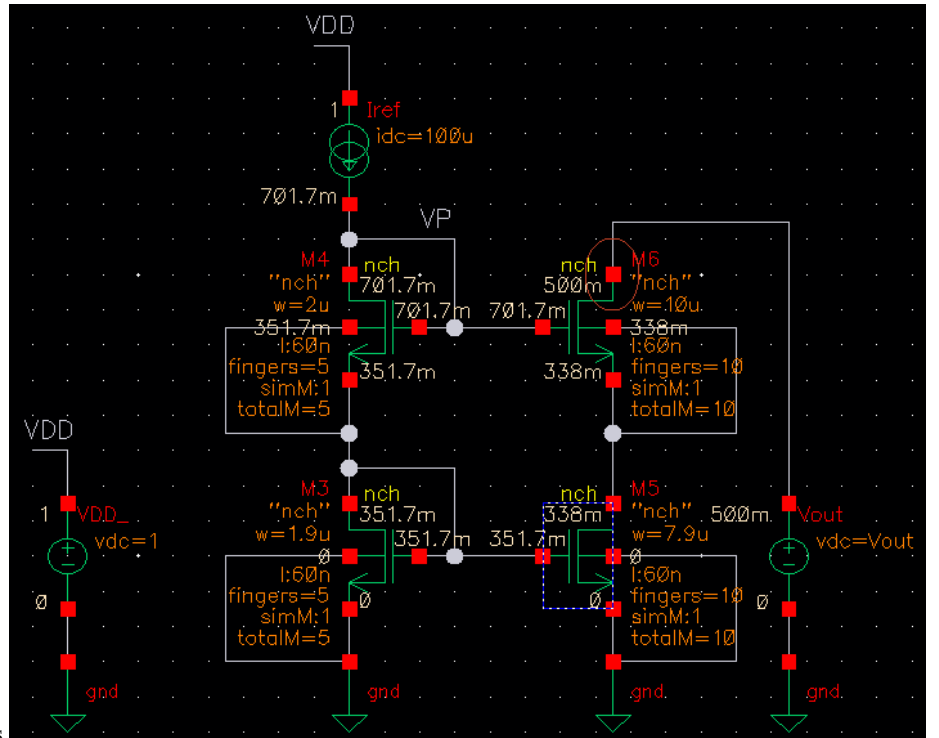


fig.(b) widths and lengths

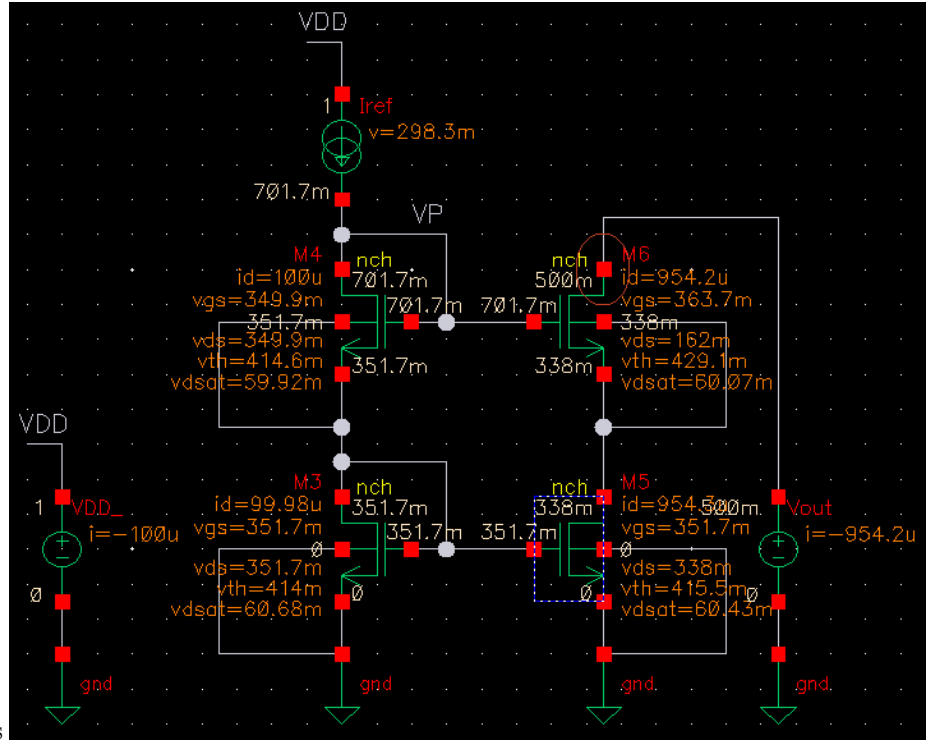


fig.(b) operating points

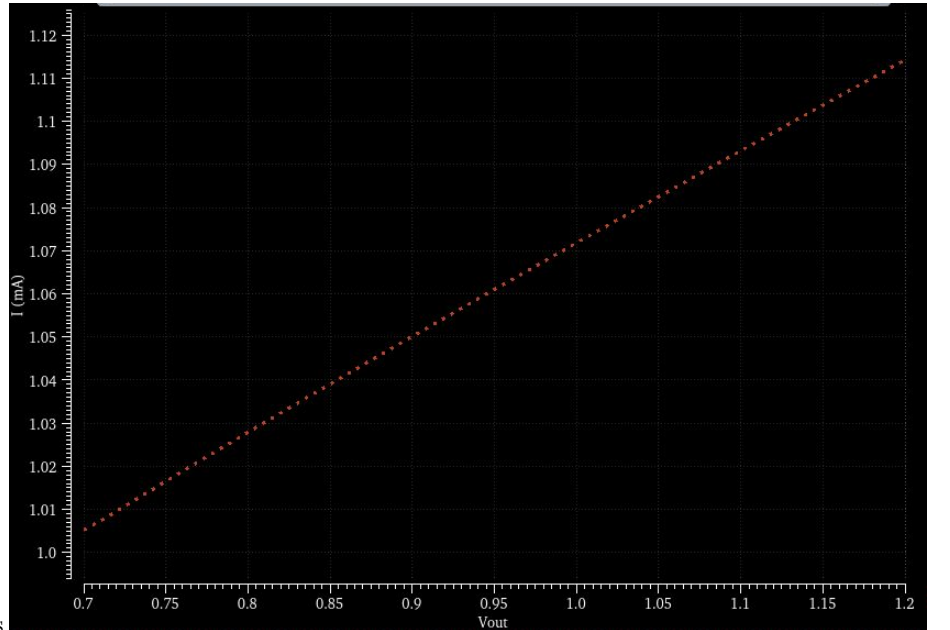


fig.(b) simulation results

$I_{out}$  varies less in fig.(b) because the output impedance is higher than fig.(a).

Higher output impedance means that the output current is less affected by the output voltage. As an ideal current source has infinite output impedance, the structure in fig.(b) is closer to an ideal current source.

## 2.5

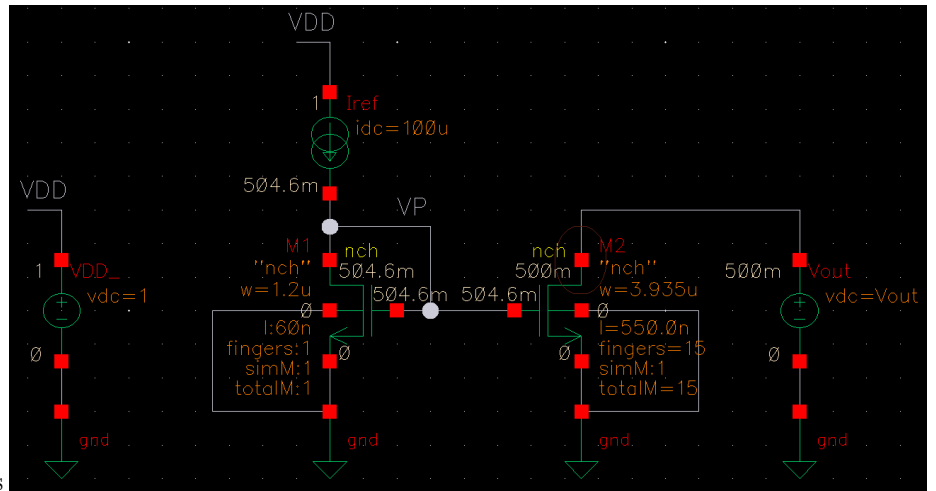


fig.(a) widths and lengths

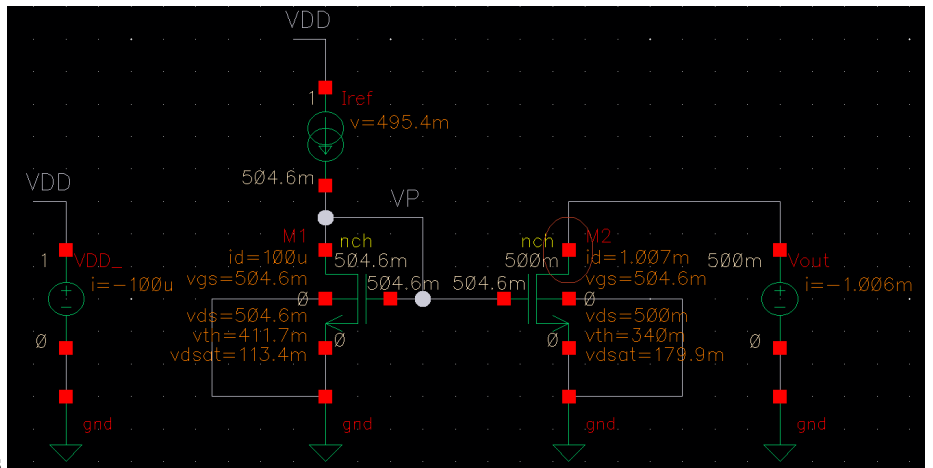


fig.(a) operating points

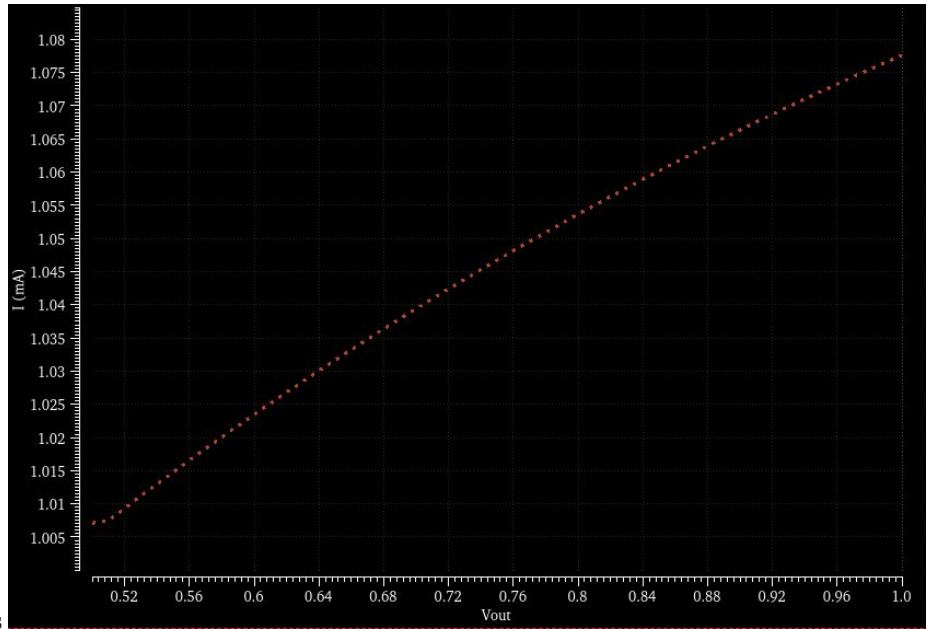


fig.(a) simulation results

## Bonus

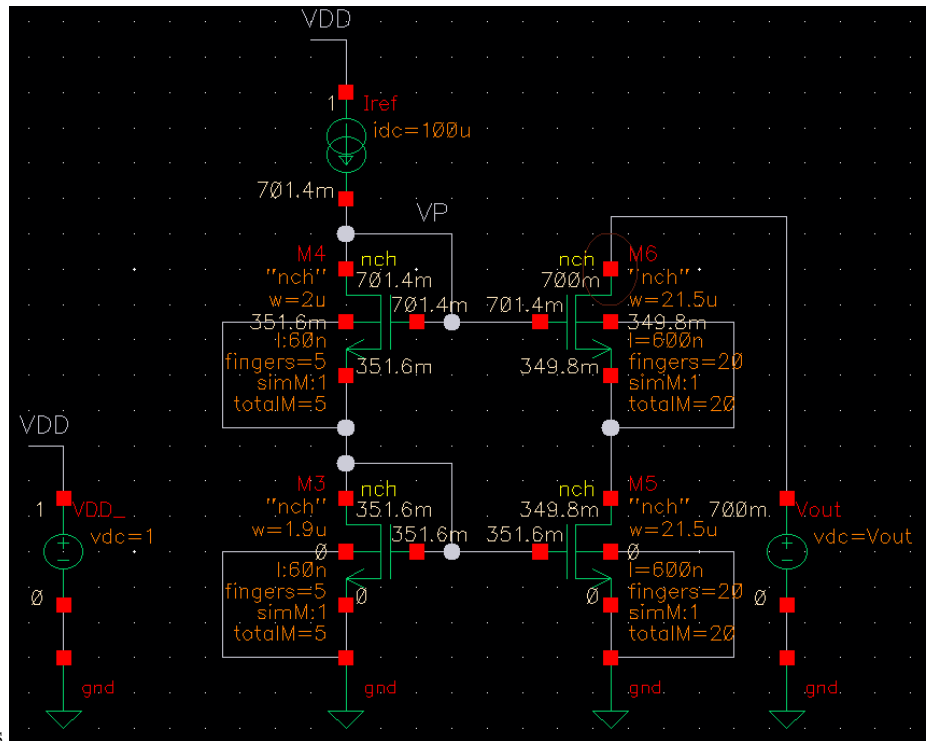


fig.(b) widths and lengths

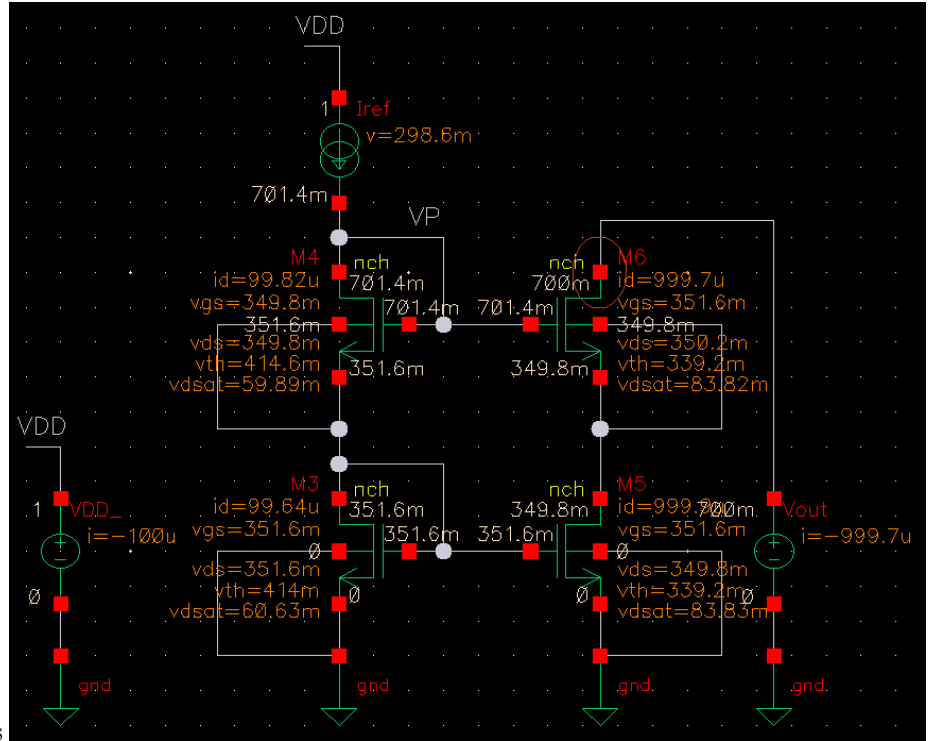


fig.(b) operating points

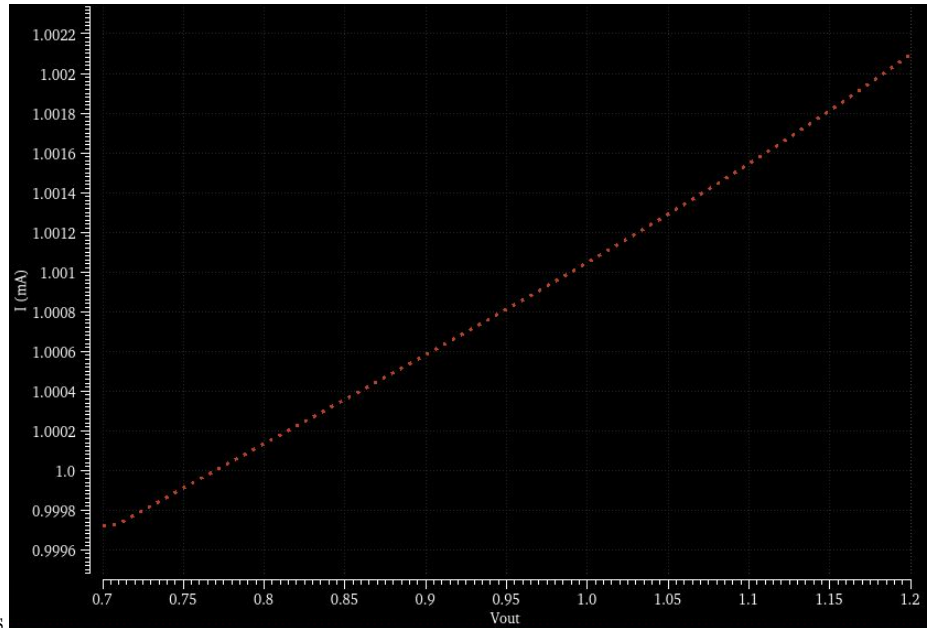


fig.(b) simulation results

I increased the output impedance by increasing the lengths of the M5 and M6

transistors. The lengths of the transistors are inversely proportional to the drain current, which is inversely proportional to the output impedance. Thus the lengths of the transistors are directly proportional to the output impedance. The higher output impedance means that the output current is less affected by the output voltage.

$$r_o = \frac{1}{\lambda I_D}, \quad I_D = \frac{1}{2} u_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$r_o = \frac{1}{\lambda \frac{1}{2} u_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}, \quad r_o \propto \frac{L}{W}$$